

NAME: ANUMITA SAMADDAR

ENROLMENT NUMBER: 2022ETB013


6TH SEMESTER





**COMPUTER ORGANISATION AND
ARCHITECTURE ASSIGNMENT**


Q) Design a 4 bit ALU that can perform the following operations:

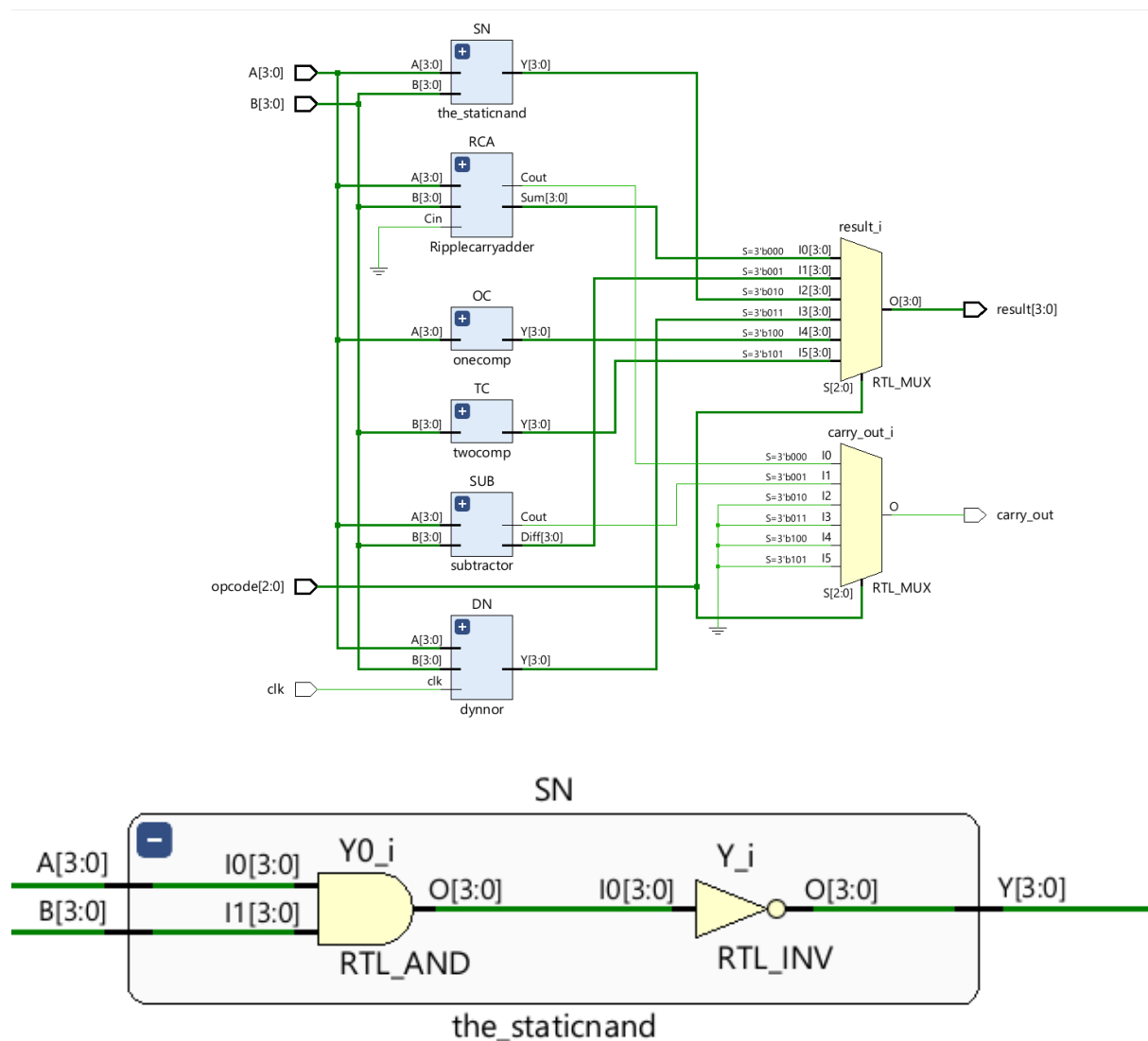- 1) 4 bit addition Opcode: 000
- 2) 4 bit subtraction Opcode: 001
- 3) 4 input Nand operation using static Nand gate Opcode: 010
- 4) 4 input Nor operation using dynamic Nor gate Opcode: 011
- 5) 1's complement of A Opcode: 100
- 6) 2's complement of B Opcode: 101

Provide schematic diagram and synthesis result.



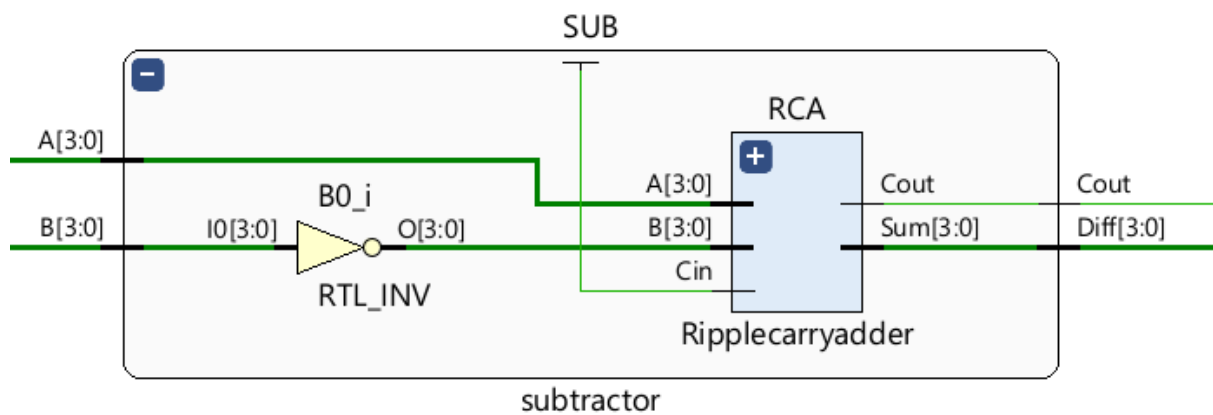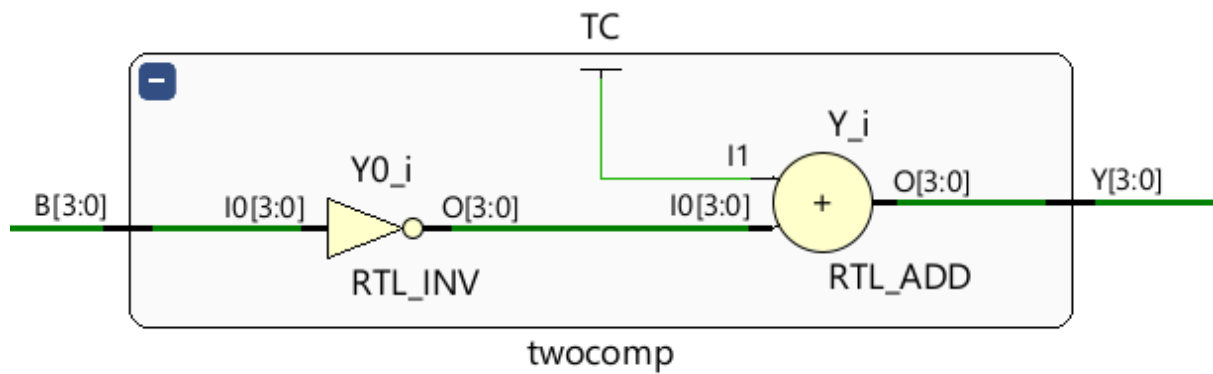 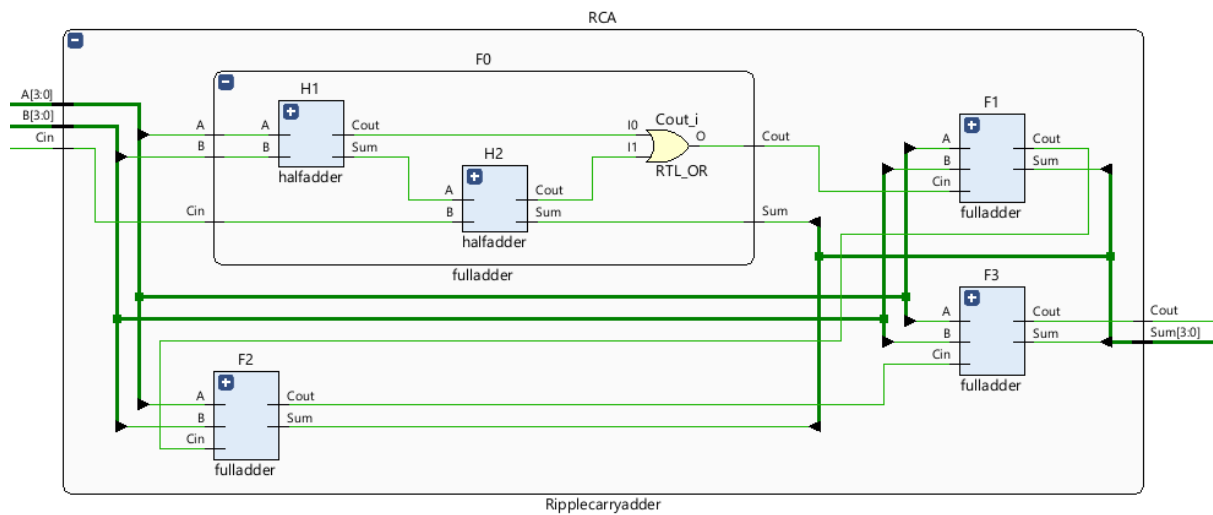

 

```

22 |
23 | module halfadder (A,B,Sum,Cout) ;
24 |     input A, B;
25 |     output Sum, Cout;
26 |     assign Sum = A ^ B;
27 |     assign Cout = A & B;
28 | endmodule
29 |
30 |
31 | module fulladder (A,B,Cin,Sum,Cout) ;
32 |     input A, B, Cin;
33 |     output Sum, Cout;
34 |     wire S1, C1, C2;
35 |     halfadder H1 (A, B, S1, C1);
36 |     halfadder H2 (S1, Cin, Sum, C2);
37 |     assign Cout = C1 | C2;
38 | endmodule
39 |
40 |
41 | module Ripplecarryadder (A,B,Cin,Sum,Cout) ;
42 |     input [3:0] A, B;
43 |     input Cin;
44 |     output [3:0] Sum;
45 |     output Cout;
46 |     wire C1, C2, C3;
47 |     fulladder F0(A[0], B[0], Cin, Sum[0], C1);
48 |     fulladder F1(A[1], B[1], C1, Sum[1], C2);
49 |     fulladder F2(A[2], B[2], C2, Sum[2], C3);
50 |     fulladder F3(A[3], B[3], C3, Sum[3], Cout);
51 | endmodule
52 |
53 |

```

```

22
23 module subtractor(A,B,Diff,Cout);
24     input [3:0] A,B;
25     output [3:0] Diff;
26     output Cout;
27     wire [3:0] B_neg;
28     Ripplecarryadder RCA(A, ~B, 1'b1, Diff, Cout);
29 endmodule
30

```

```

22
23 module the_staticnand(A,B,Y);
24     input [3:0] A, B;
25     output [3:0] Y;
26     assign Y = ~(A & B);
27 endmodule
28

```

```

22
23 module dynnor(A,B,clk,Y);
24     input [3:0] A, B;
25     input clk; // Clock controls dynamic phases
26     output [3:0] Y;
27     // clk=0 -> precharge phase
28     // clk=1 -> evaluate phase
29     assign Y = (clk == 1'b0) ? 4'b1111 : ~(A | B);
30 endmodule
31
32

```

```

22
23 module onecomp(A,Y);
24     input [3:0] A;
25     output [3:0] Y;
26     assign Y = ~A;
27 endmodule
28

```

```

21
22 module twocomp(B,Y);
23     input [3:0] B;
24     output [3:0] Y;
25     assign Y = ~B + 1;
26 endmodule
27

```

```

23 module ALU_4bit (A,B,opcode,clk,result,carry_out);
24     input [3:0] A, B;
25     input [2:0] opcode;
26     input clk;           // Clock-> dynamic nor
27     output reg [3:0] result;
28     output reg carry_out;
29
30     wire [3:0] sum, diff, nand_out, nor_out, ones_comp, twos_comp;
31     wire sum_cout, diff_cout;
32
33     Ripplecarryadder RCA (.A(A), .B(B), .Cin(1'b0), .Sum(sum), .Cout(sum_cout));
34     subtractor SUB (.A(A), .B(B), .Diff(diff), .Cout(diff_cout));
35     the_staticnand SN (.A(A), .B(B), .Y(nand_out));
36     dynnor DN (.A(A), .B(B), .clk(clk), .Y(nor_out));
37     onecomp OC (.A(A), .Y(ones_comp));
38     twocomp TC (.B(B), .Y(twos_comp));
39
40     always @(*) begin
41         case (opcode)
42             3'b000: begin
43                 result = sum;
44                 carry_out = sum_cout;
45             end
46             3'b001: begin
47                 result = diff;
48                 carry_out = diff_cout;
49             end
50             3'b010: begin
51                 result = nand_out;
52                 carry_out = 0;
53             end
54             3'b011: begin
55                 result = nor_out;
56                 carry_out = 0;
57             end
58             3'b100: begin
59                 result = ones_comp;
60                 carry_out = 0;
61             end
62             3'b101: begin

```

```

61         end
62         3'b101: begin
63             result = twos_comp;
64             carry_out = 0;
65         end
66         default: begin
67             result = 4'bxxxx;
68             carry_out = 1'bx;
69         end
70     endcase
71 end
72 endmodule
73

```

```

20 module ALU_4bit_tb;
21     // Inputs
22     reg [3:0] A;
23     reg [3:0] B;
24     reg [2:0] opcode;
25     reg clk;
26
27     // Outputs
28     wire [3:0] result;
29     wire carry_out;
30
31
32     ALU_4bit uut (.A(A), .B(B), .opcode(opcode), .clk(clk), .result(result), .carry_out(carry_out));
33
34     // (10 ns period)
35     initial begin
36         clk = 0;
37         forever #5 clk = ~clk;
38     end
39
40
41     initial begin
42         // Initial state
43         A = 4'b0000; B = 4'b0000; opcode = 3'b000; #10;
44
45
46         A = 4'b1001;
47         B = 4'b0101;
48         opcode = 3'b000;
49         #10;
50
51         A = 4'b1100;
52         B = 4'b0111;
53         opcode = 3'b001;
54         #10;
55
56
57         A = 4'b1010;
58         B = 4'b1100;
59         opcode = 3'b010;

```

```

44
45
46 ○ A = 4'b1001;
47 ○ B = 4'b0101;
48 ○ opcode = 3'b000;
49 ○ #10;
50
51 ○ A = 4'b1100;
52 ○ B = 4'b0111;
53 ○ opcode = 3'b001;
54 ○ #10;
55
56
57 ○ A = 4'b1010;
58 ○ B = 4'b1100;
59 ○ opcode = 3'b010;
60 ○ #10;
61
62 ○ A = 4'b1001;
63 ○ B = 4'b0110;
64 ○ opcode = 3'b011;
65 ○ #20;
66
67 ○ A = 4'b1111;
68 ○ opcode = 3'b100;
69 ○ #10;
70
71 ○ B = 4'b0010;
72 ○ opcode = 3'b101;
73 ○ #10;
74
75 ○ → $finish;
76 △ end
77
78 △ initial begin
79 ○ $monitor("Time=%0t | clk=%b | opcode=%b | A=%b | B=%b | result=%b | carry_out=%b",
80 $time, clk, opcode, A, B, result, carry_out);
81 △ end
82 △ endmodule
83
84

```

```
# run 1000ns
```

```

Time=0 | clk=0 | opcode=000 | A=0000 | B=0000 | result=0000 | carry_out=0
Time=5000 | clk=1 | opcode=000 | A=0000 | B=0000 | result=0000 | carry_out=0
Time=10000 | clk=0 | opcode=000 | A=1001 | B=0101 | result=1110 | carry_out=0
Time=15000 | clk=1 | opcode=000 | A=1001 | B=0101 | result=1110 | carry_out=0
Time=20000 | clk=0 | opcode=001 | A=1100 | B=0111 | result=0101 | carry_out=1
Time=25000 | clk=1 | opcode=001 | A=1100 | B=0111 | result=0101 | carry_out=1
Time=30000 | clk=0 | opcode=010 | A=1010 | B=1100 | result=0111 | carry_out=0
Time=35000 | clk=1 | opcode=010 | A=1010 | B=1100 | result=0111 | carry_out=0
Time=40000 | clk=0 | opcode=011 | A=1001 | B=0110 | result=1111 | carry_out=0
Time=45000 | clk=1 | opcode=011 | A=1001 | B=0110 | result=0000 | carry_out=0
Time=50000 | clk=0 | opcode=011 | A=1001 | B=0110 | result=1111 | carry_out=0
Time=55000 | clk=1 | opcode=011 | A=1001 | B=0110 | result=0000 | carry_out=0
Time=60000 | clk=0 | opcode=100 | A=1111 | B=0110 | result=0000 | carry_out=0
Time=65000 | clk=1 | opcode=100 | A=1111 | B=0110 | result=0000 | carry_out=0
Time=70000 | clk=0 | opcode=101 | A=1111 | B=0010 | result=1110 | carry_out=0
Time=75000 | clk=1 | opcode=101 | A=1111 | B=0010 | result=1110 | carry_out=0
$finish called at time : 80 ns : File "C:/Users/Anumita Samaddar/ALU4bit anumita/

```